

Counters & Registers

Electrical Engineering

The sequential building blocks, sorted by clocking and by what they hold.

Same flip-flops, arranged for counting or for storage.

Counters

Ripple: each stage clocks the next one

Synchronous: one clock reaches every stage

Modulo-n: decode the count and reset

Up or down: direction from a control input

Ring and Johnson: shift-based sequences

Registers

Parallel load: every bit on one edge

Shift: serial in, serial out

Serial in, parallel out deserialises

Universal: load, shift either way, or hold

A shift register also divides frequency

Ripple counter outputs are skewed by accumulated delay, so decoding one produces glitches a synchronous counter would not.