

Driving Loads

Electrical Engineering

Getting from a logic pin to a relay, motor or solenoid it could never drive directly.

The pin cannot supply the current, and the coil will fight back.

1 Check the pin's limits

A GPIO sources tens of milliamps, and the whole port has its own limit.

2 Pick the switching device

A logic-level MOSFET for DC loads, or a relay where isolation is needed.

3 Condition the gate

A series resistor limits inrush; a pull-down holds the gate off at reset.

4 Clamp the inductive kick

A flyback diode across the coil catches the reverse voltage spike.

5 Separate the grounds

Return load current on its own path and join the grounds at one point.

Educational reference. Mains-voltage loads need isolation, enclosure and qualified supervision under local electrical regulations.