

Op-Amp Non-Idealities

Electrical Engineering

What the datasheet is warning about, sorted into DC errors and frequency limits.

The ideal op-amp fails in two distinct directions.

DC errors

Input offset voltage shifts the output

Bias current across high-value resistors

Offset drift as the part warms up

Finite CMRR lets common mode leak through

Output cannot reach either supply rail

AC limits

Gain-bandwidth product caps usable gain

Slew rate limits large fast signals

Capacitive loads eat the phase margin

Input noise density sets the noise floor

Settling time outlasts the rise time

Two limits look alike on a scope: slew rate flattens the edges of a big signal, bandwidth merely rounds a small one.