

Small-Signal Models

Electrical Engineering

Linearising a transistor around its bias point, and what transconductance actually is.

Around a bias point a nonlinear device behaves linearly, described by its transconductance.

BJT: $g_m = I_C/V_T$ · FET: $g_m = 2I_D/V_{ov}$

$I_C = 1\text{ mA}$

$1\text{ mA} \div 26\text{ mV}$.

$g_m \approx 38\text{ mS}$

$\beta = 100$

$\beta \div g_m$.

$r_\pi \approx 2.6\text{ k}\Omega$

$R_C = 1\text{ k}\Omega$

Bias sets gain.

Gain ≈ -38

THE COMMON MISTAKE

✗ Using the small-signal model for a large swing

✓ Keeping the signal well below the bias

The model is the first term of a Taylor expansion. Drive it hard and the terms you dropped return as distortion and clipping.

To draw the small-signal circuit, kill the DC: supply rails become ground and bias current sources become open circuits.