

# Zener Regulator

Electrical Engineering

Sizing the series resistor for a shunt regulator, worst case at both extremes.

*The resistor must satisfy the two opposite corners at once.*

## 1 Fix the zener voltage

Choose  $V_Z$  at the output you need and note its test current  $I_{ZT}$ .

## 2 Take the tight corner

Lowest input voltage with the highest load current is the binding case.

## 3 Size the series resistor

$R = (V_{in\ min} - V_Z) / (I_{load\ max} + I_{Z\ min})$ ; keep  $I_Z$  min near 5 mA.

## 4 Check the other corner

Highest input with no load at all: the zener then carries every milliamp.

## 5 Check dissipation

$P_Z = V_Z I_{Z\ max}$  and  $P_R = (V_{in} - V_Z)^2 / R$ . Derate both parts.

A shunt regulator draws its full current whether the load needs it or not. Past about 100 mW, use a series regulator.